

ECE111|Digital Circuits  
Dr. Vish Visweswaran  
Lab\_4:


Student Name : Shivam Agarwal  
Roll No. : 2020123  
Date : 12/2/2021

---

### **Aim 1: Design a 2x1 MUX using basic GATES**

**Components/ICs Use:** 1 power supply, 3 slide switches, 4 resistors (1kohm), 4 LED, 1 Quad AND gate , 1 Quad OR gate, 1 Hex Inverter

### **Circuit Diagram:**

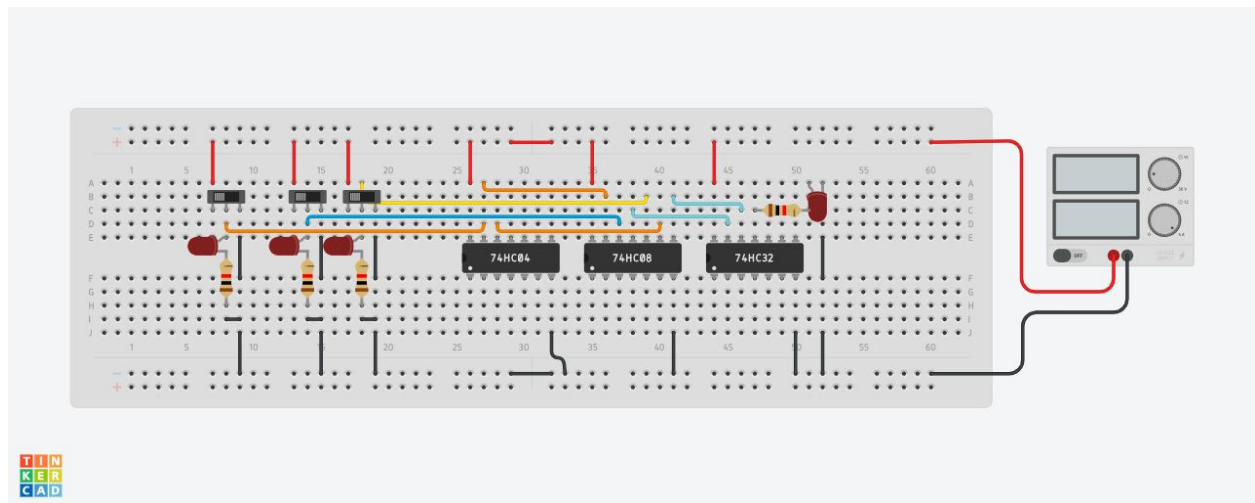

**Link of TINKERCAD Workspace:**


[https://www.tinkercad.com/things/ctkA3LWDZD6-brilliant-robo-luulia/editel?sharecode=0quTkyTYoGmWxaN3XofEWB1Q-j\\_jA438nA\\_DbAtL4N8](https://www.tinkercad.com/things/ctkA3LWDZD6-brilliant-robo-luulia/editel?sharecode=0quTkyTYoGmWxaN3XofEWB1Q-j_jA438nA_DbAtL4N8)

**Truth Table:**

S	Output
---	--------

0	i0
1	i1

**Logic circuit diagram:**

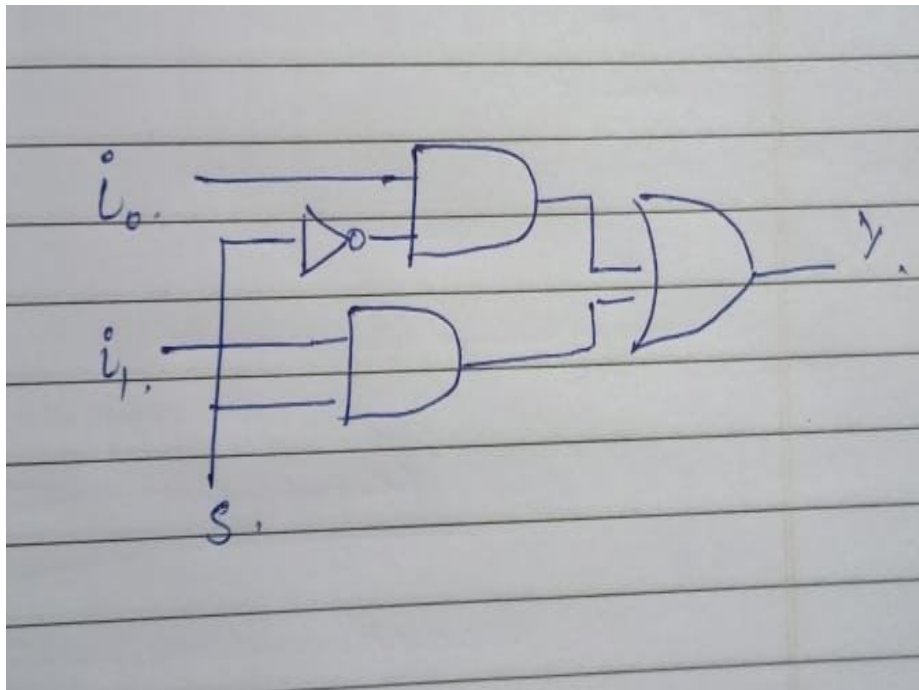

**Observations/Results:**

When the value of  $s$  is 0 the  $i_0$  is given as output however when  $s$  is 1 then  $i_1$  is given as output.


**Applications of the 2x1 MUX**

- 1) It is used to connect 2 data lines to the output and send only one of them on the basis of selection signal
- 2) Can be used to create higher degree mux like 4x1 MUX by using several 2x1 MUX together

## Aim 2: Design a 4x1 MUX using basic GATES

**Components/ICs Use:** 1 power supply, 6 slide switches, 7 resistors (1kohm), 7 LED, 2 Triple AND gate , 1 Quad OR gate, 1 Hex Inverter

### **Circuit Diagram:**

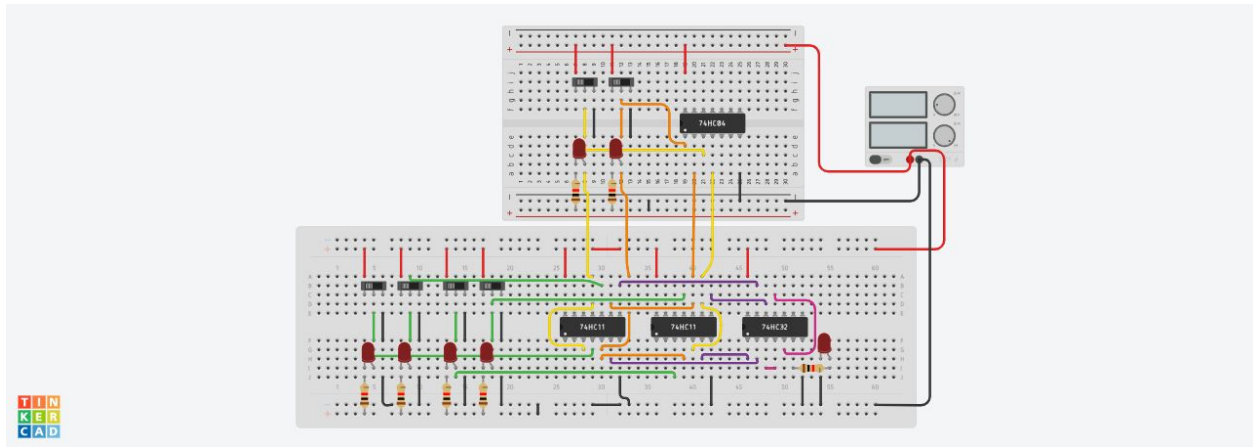


### **Link of TINKERCAD Workspace:**

<https://www.tinkercad.com/things/9m6IJPFm3NB-copy-of-2x1-mux/editel?sharecode=9SBCct6NFtACRkoM72fZVXxD-c62BQK7uVKbSUYfm2U>

### **Truth Table:**

s1	s0	Output
0	0	i0
0	1	i1
1	0	i2
1	1	i3

**Logic circuit diagram:**

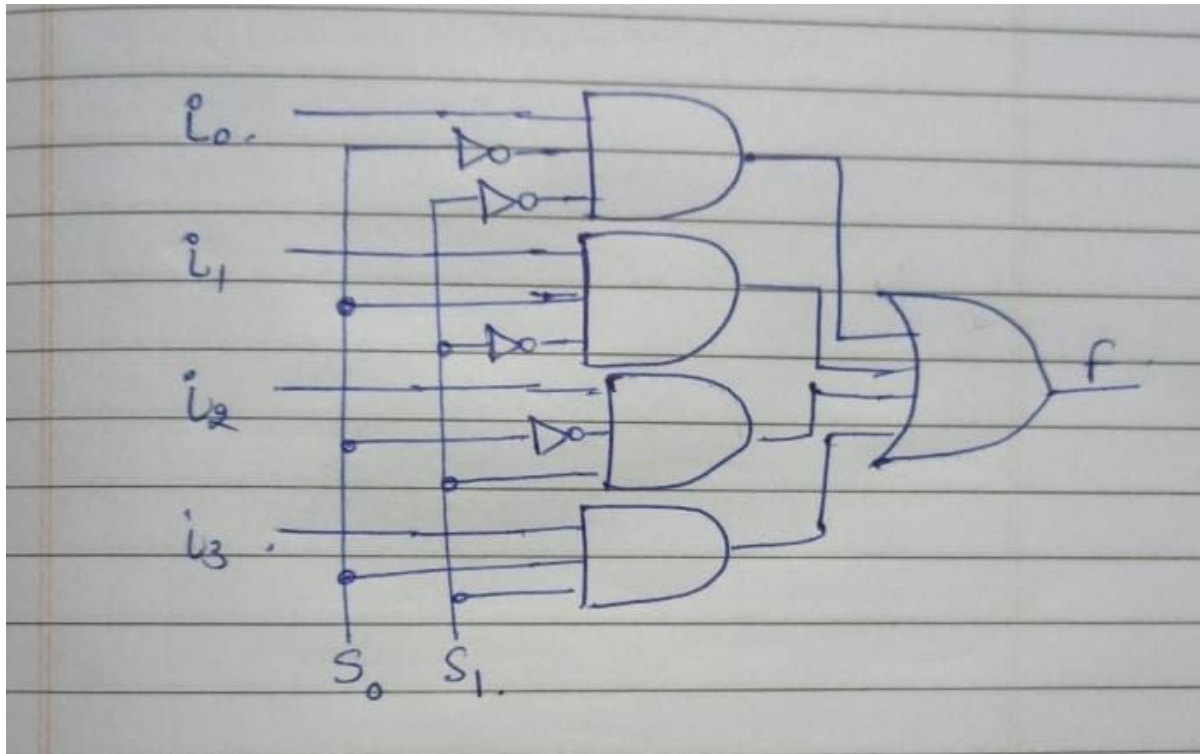

**Observations/Results:**

From the given experiment we can prove that :

$$F = s1'.s0'.i0 + s1'.s0.i1 + s1.s0'.i2 + s1.s0.i3$$


### **Applications of the 4x1 MUX**

- 1) It is used to give a single output from 4 input lines based on the selection signal
- 2) It is a good method for data routing

### **Aim 3: Design a 8x1 MUX using basic GATES**

**Components/ICs Use:** 1 power supply, 11 slide switches, 12 resistors (1kohm), 12 LED, 4 dual AND gate , 2 Quad OR gate, 1 Hex Inverter

## Circuit Diagram:

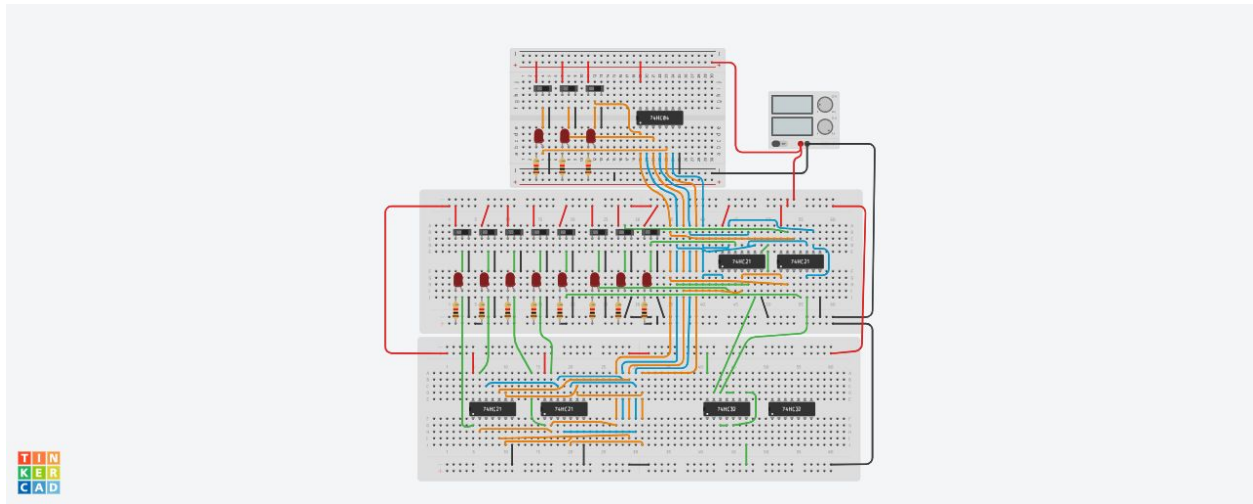

## Link of TINKERCAD Workspace:


<https://www.tinkercad.com/things/0jprE5VafuR-copy-of-4x1-mux/editel?sharecode=Uh16yMK133q-e5DPvC8DrmJOLMD4U8853gcR5JPnNV4>

## Truth Table:

s2	s1	s0	Output
0	0	0	i0
0	0	1	i1
0	1	0	i2
0	1	1	i3
1	0	0	i4
1	0	1	i5
1	1	0	i6
1	1	1	i7



Logic circuit diagram:

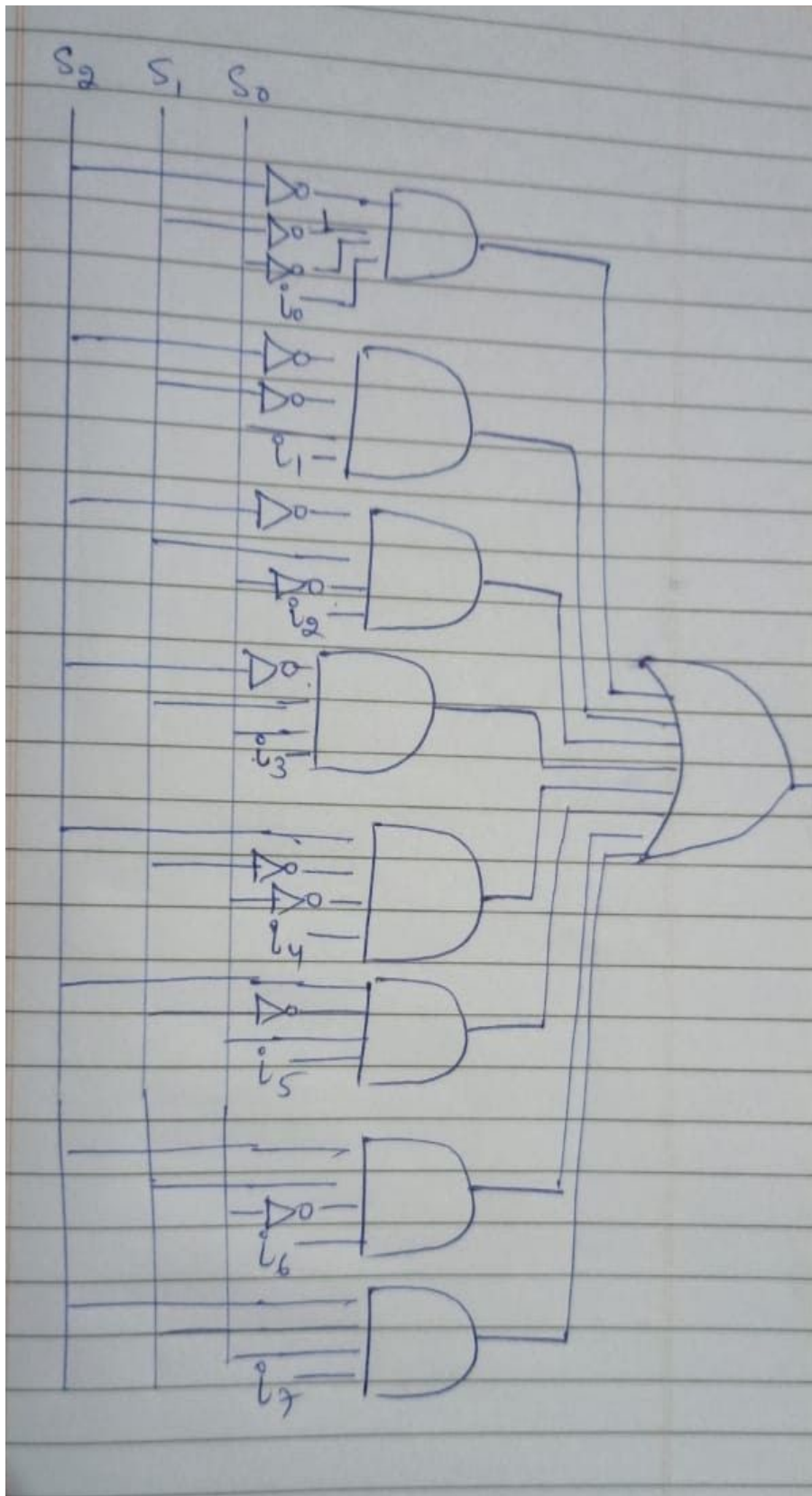

### **Observations/Results:**

From the given experiment we can prove that :

$$F = s_2'.s_1'.s_0'.i_0 + s_2'.s_1'.s_0.i_1 + s_2'.s_1.s_0'.i_2 + s_2'.s_1.s_0.i_3 + s_2.s_1'.s_0'.i_4 + s_2.s_1'.s_0.i_5 + s_2.s_1.s_0'.i_6 + s_2.s_1.s_0.i_7$$

### **Applications of the 8x1 MUX**

- 1) It is used to to give a single output from 8 input lines based on the selection signal
- 2) It is useful in parallel data transmission