

**ECE111|Digital Circuits**

**Dr. Vish Visweswaran**

**Lab\_5:**

**Student Name : Shivam Agarwal**

**Roll No. : 2020123**


**Date : 07/3/2021**

---

**Aim 1 : Implement a 7 segment decoder using CD 4511 IC**

**Components / ICs used** : 1 power supply , 4 slide switches , 1 7-Segment Decoder , 1 Cathode 7-Segment Display , 7 1kohm resistors


**Circuit Diagram :**

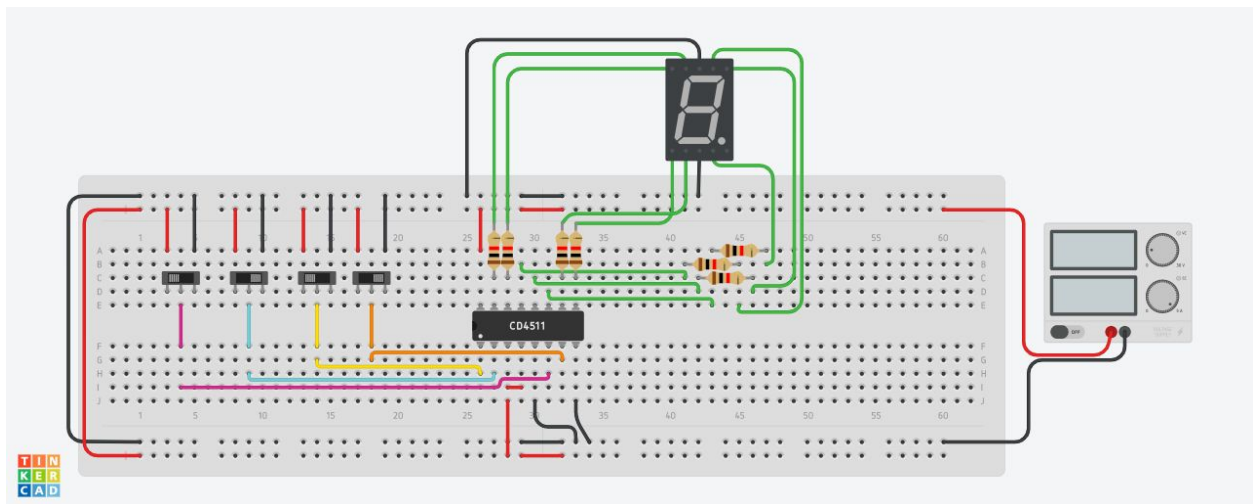

**Link of Tinkercad workspace :**

[https://www.tinkercad.com/things/k45AkXYK62F-7-segment-display/editel?sharecode=StUUVZafPzcsKaoZ-3\\_-e\\_pY52O1MAJ\\_64170ajtwDQ](https://www.tinkercad.com/things/k45AkXYK62F-7-segment-display/editel?sharecode=StUUVZafPzcsKaoZ-3_-e_pY52O1MAJ_64170ajtwDQ)


## IC - CD4511

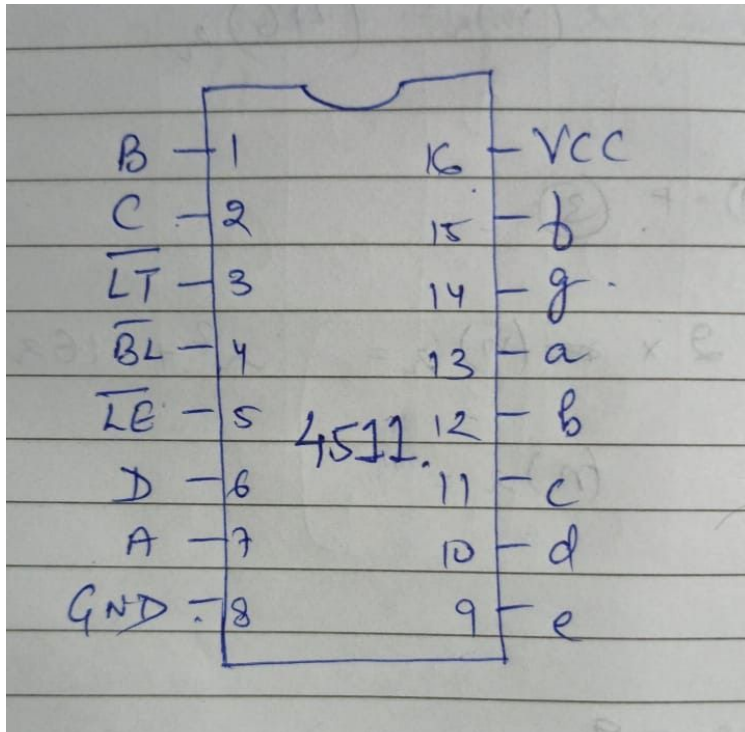

Truth Table :

DE	D	C	B	A	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	0	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	0	1	1

## Logic Circuit Diagram :

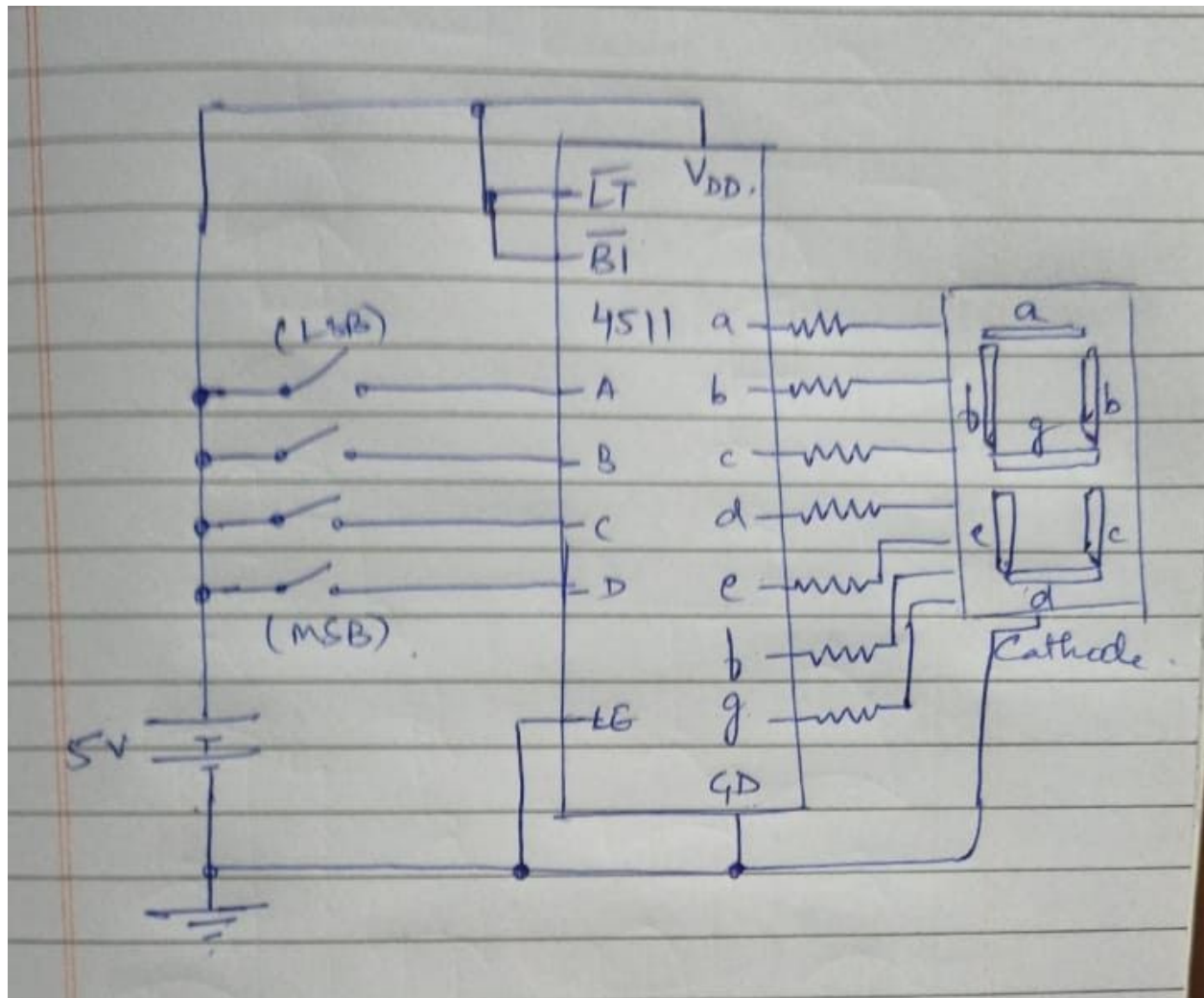


## Observations :

The 7 segment display displays the decimal equivalent of the input DCBA which is in the form of BCD(Binary Coded Decimal)

## **Aim 1 : Implement a 7 segment decoder by only using basic gates**

**Components / ICs used :** 1 power supply , 4 slide switches , 1hex inverter , 1 Cathode 7-Segment Display , 4 1kohm resistors, 6 Quad and gate , 6 Quad or gate

### **Circuit Diagram :**

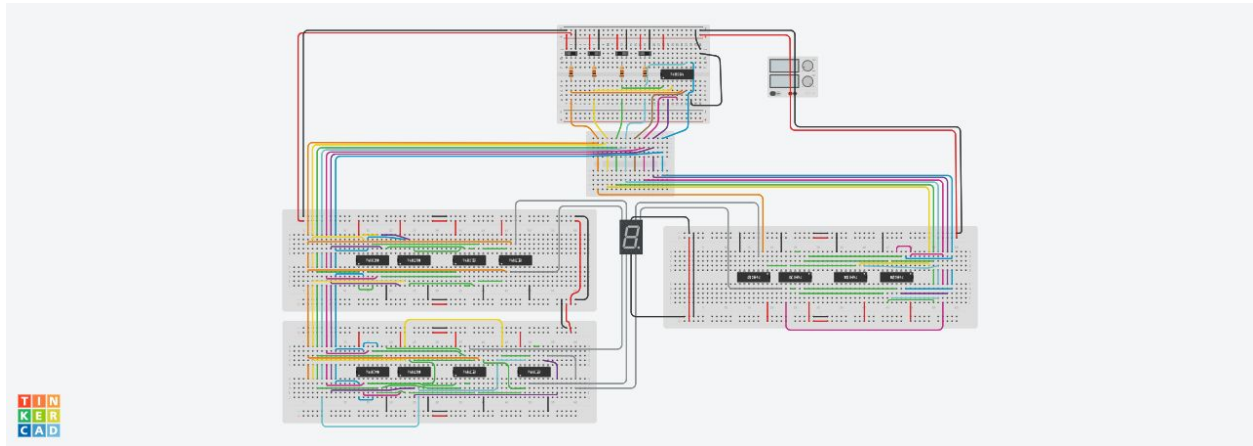

### **Link of Tinkercad workspace :**

[https://www.tinkercad.com/things/0fbMpDMM4Hk-copy-of-7-segment-display-using-basic-gates/editel?sharecode=bvCDWbC7m2l6mlkypnQW3X\\_t9EI5AGLmyJj01OHVaKs](https://www.tinkercad.com/things/0fbMpDMM4Hk-copy-of-7-segment-display-using-basic-gates/editel?sharecode=bvCDWbC7m2l6mlkypnQW3X_t9EI5AGLmyJj01OHVaKs)

K maps :


KMap for a.



$$a = D + \bar{C}B + AC + \bar{D}\bar{C}\bar{A}$$

$$= D + \bar{B}\bar{B}\bar{C} + AC + \bar{C}\bar{A}$$


KMap for b.

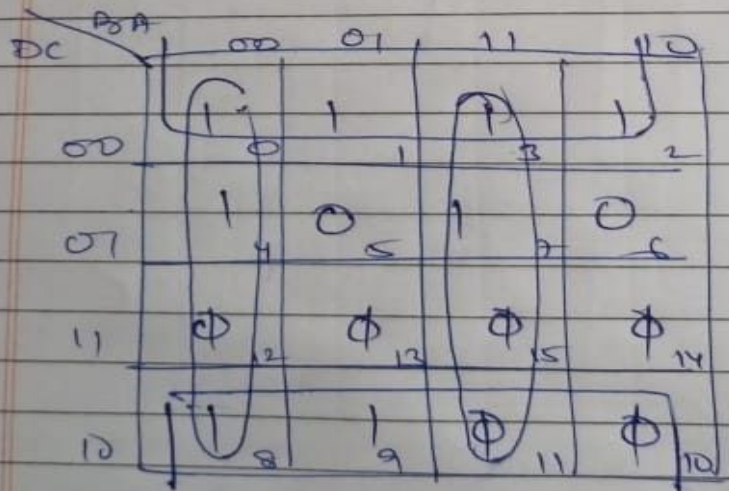

$$b = \bar{C} + \bar{A}\bar{B} + AB$$




KMap for c

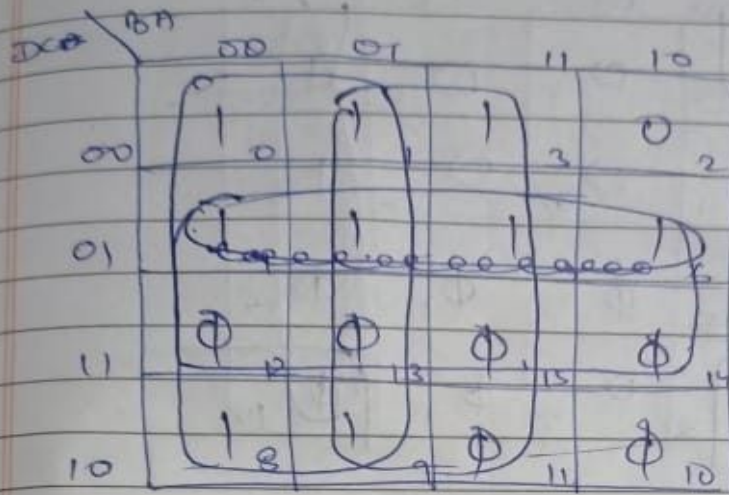

$$c = \bar{B} + A + C$$

~~⊗~~

KMap for d.

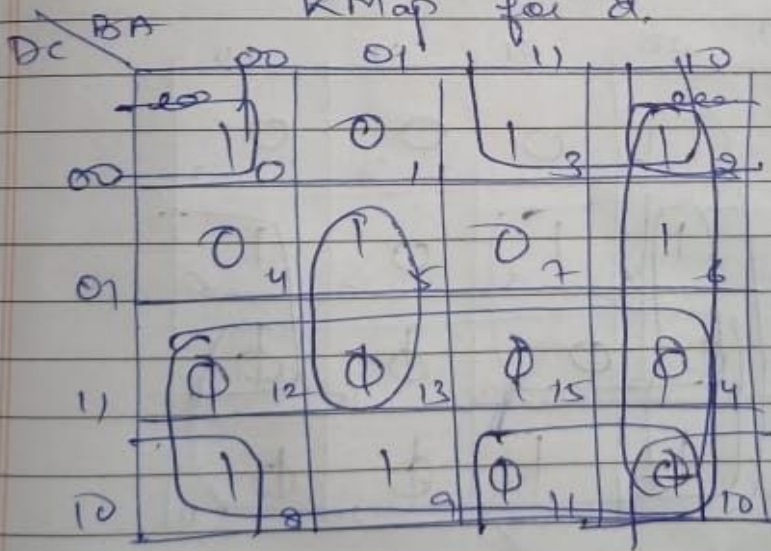

$$d = D + \bar{B}A + \bar{C}B + \bar{C}\bar{A} + C\bar{B}A$$

$$= D + \bar{B}A + \bar{C}B + \bar{C}\bar{A} + \bar{A}BC$$

Kmap for e

DC \ AB	00	01	11	10
00	1 <sub>0</sub>	0 <sub>1</sub>	0 <sub>3</sub>	1 <sub>2</sub>
01	0 <sub>4</sub>	0 <sub>5</sub>	0 <sub>7</sub>	1 <sub>6</sub>
11	0 <sub>12</sub>	0 <sub>13</sub>	0 <sub>15</sub>	0 <sub>14</sub>
10	1 <sub>8</sub>	0 <sub>9</sub>	0 <sub>11</sub>	0 <sub>10</sub>


$$e = \bar{A}B + \bar{A}\bar{C}$$

Kmap for f

DC \ AB	00	01	11	10
00	1 <sub>0</sub>	0 <sub>1</sub>	0 <sub>3</sub>	0 <sub>2</sub>
01	1 <sub>4</sub>	1 <sub>5</sub>	0 <sub>7</sub>	1 <sub>6</sub>
11	0 <sub>12</sub>	0 <sub>13</sub>	0 <sub>15</sub>	0 <sub>14</sub>
10	1 <sub>8</sub>	1 <sub>9</sub>	0 <sub>11</sub>	0 <sub>10</sub>

$$f = D + C\bar{A} + C\bar{B} + \bar{A}\bar{B}$$


Kmap for  $g$ .

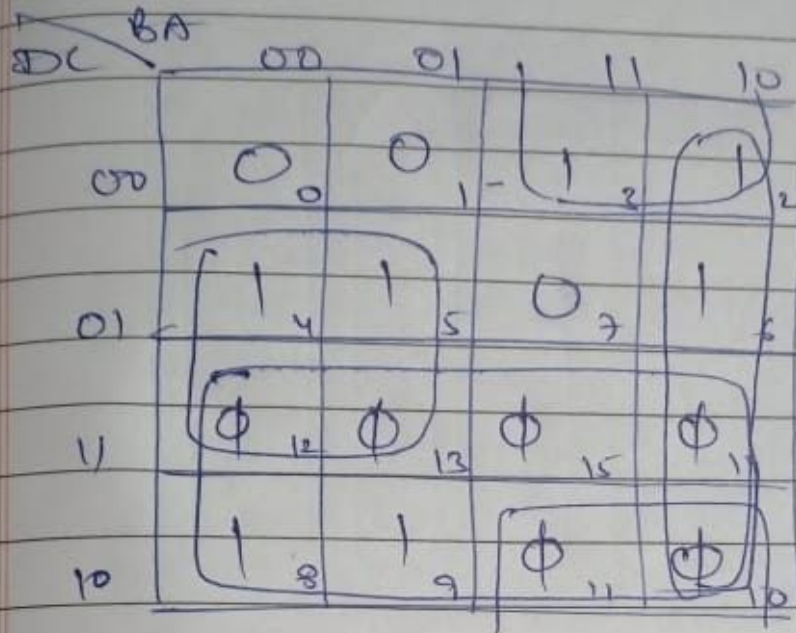


$$g = D + C \cdot \bar{B} + \bar{C} \cdot B + \bar{A} B$$




## Logic Circuit Diagrams :

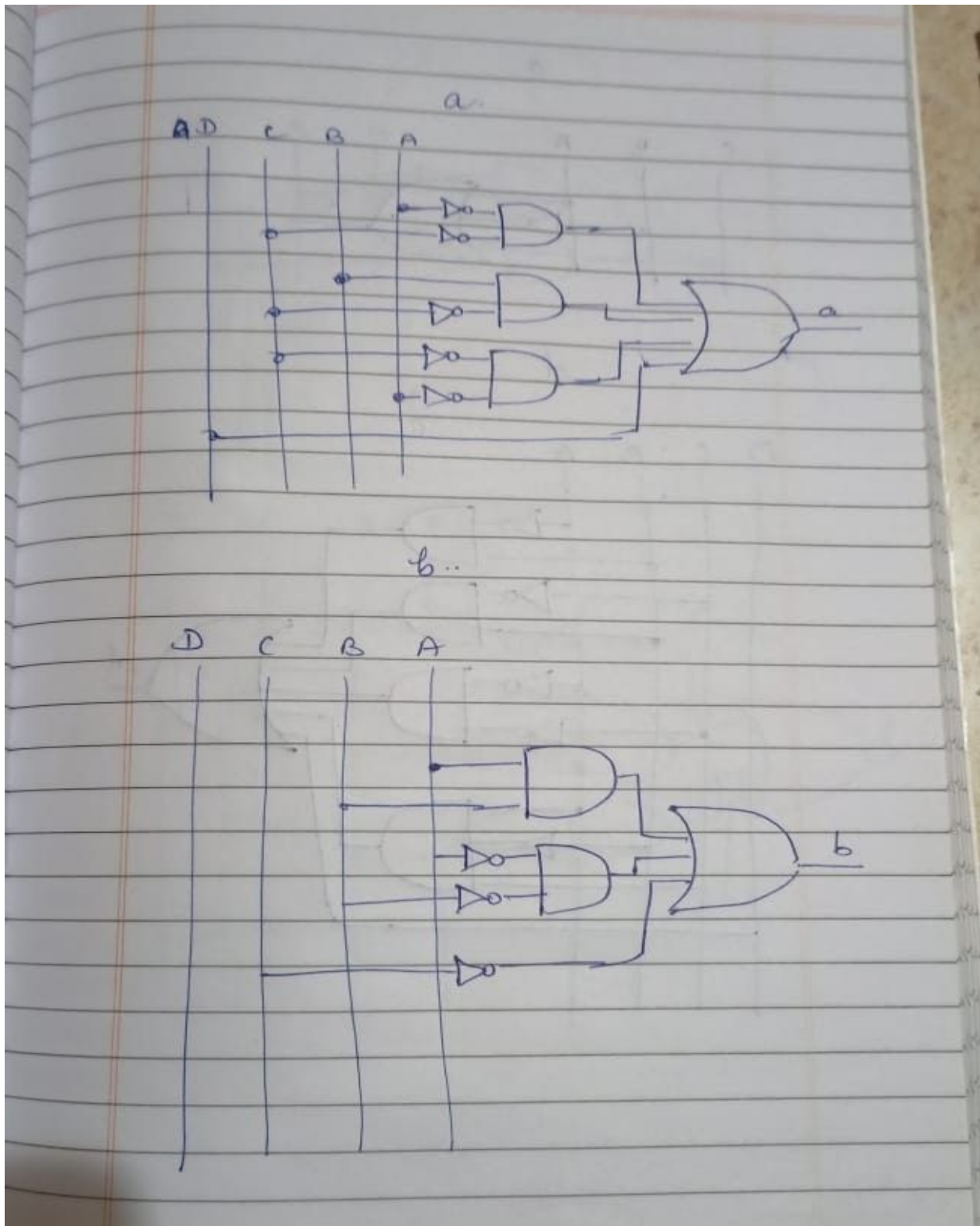


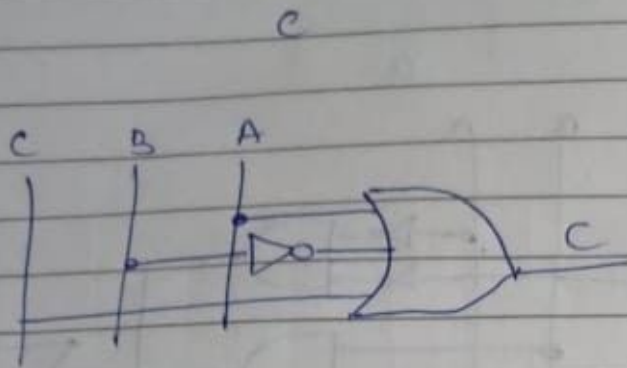


d.

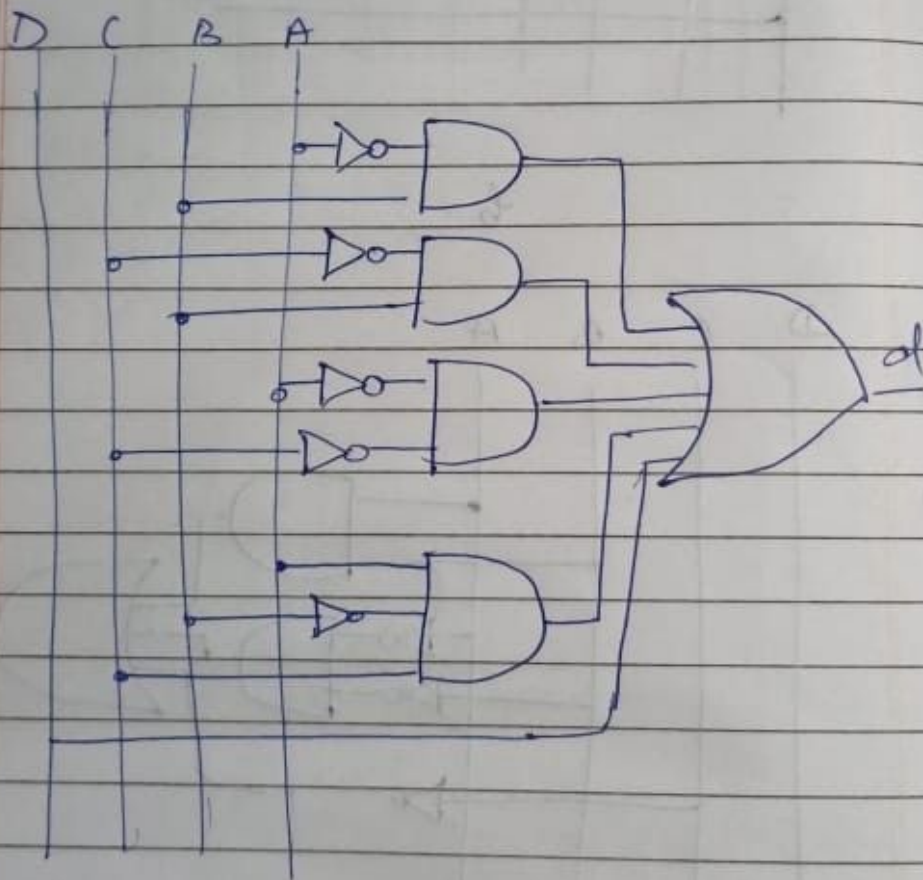


e.

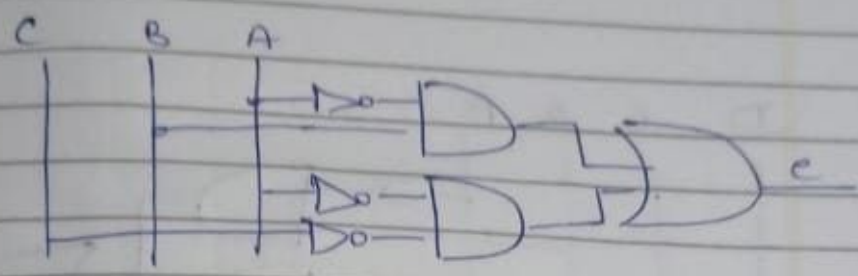

f.

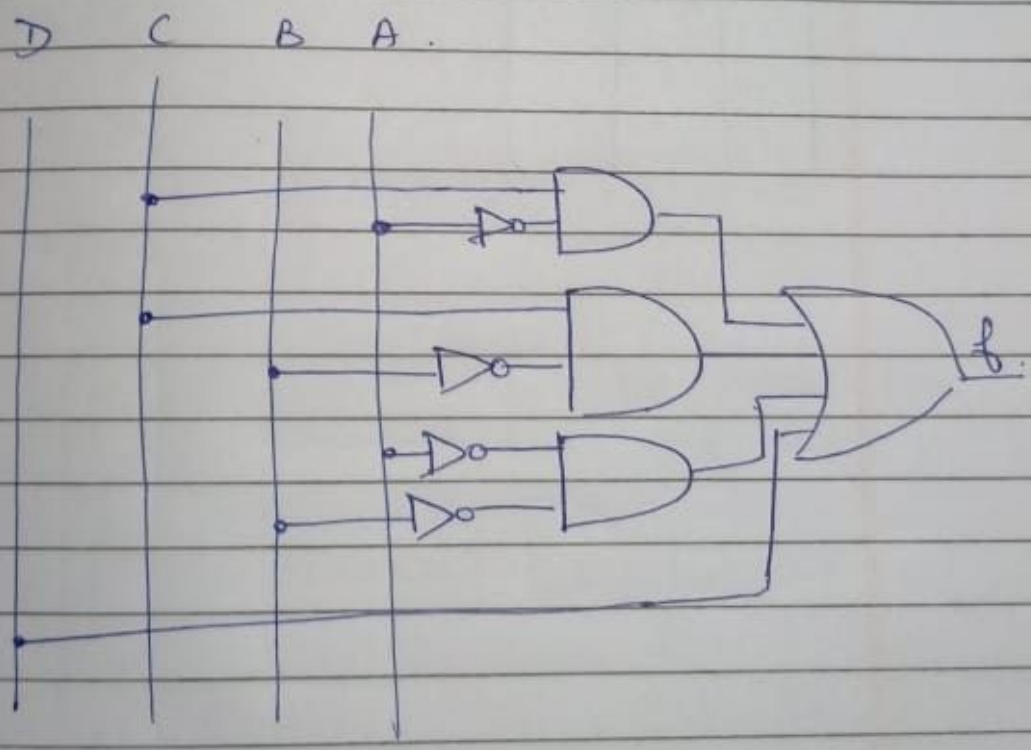

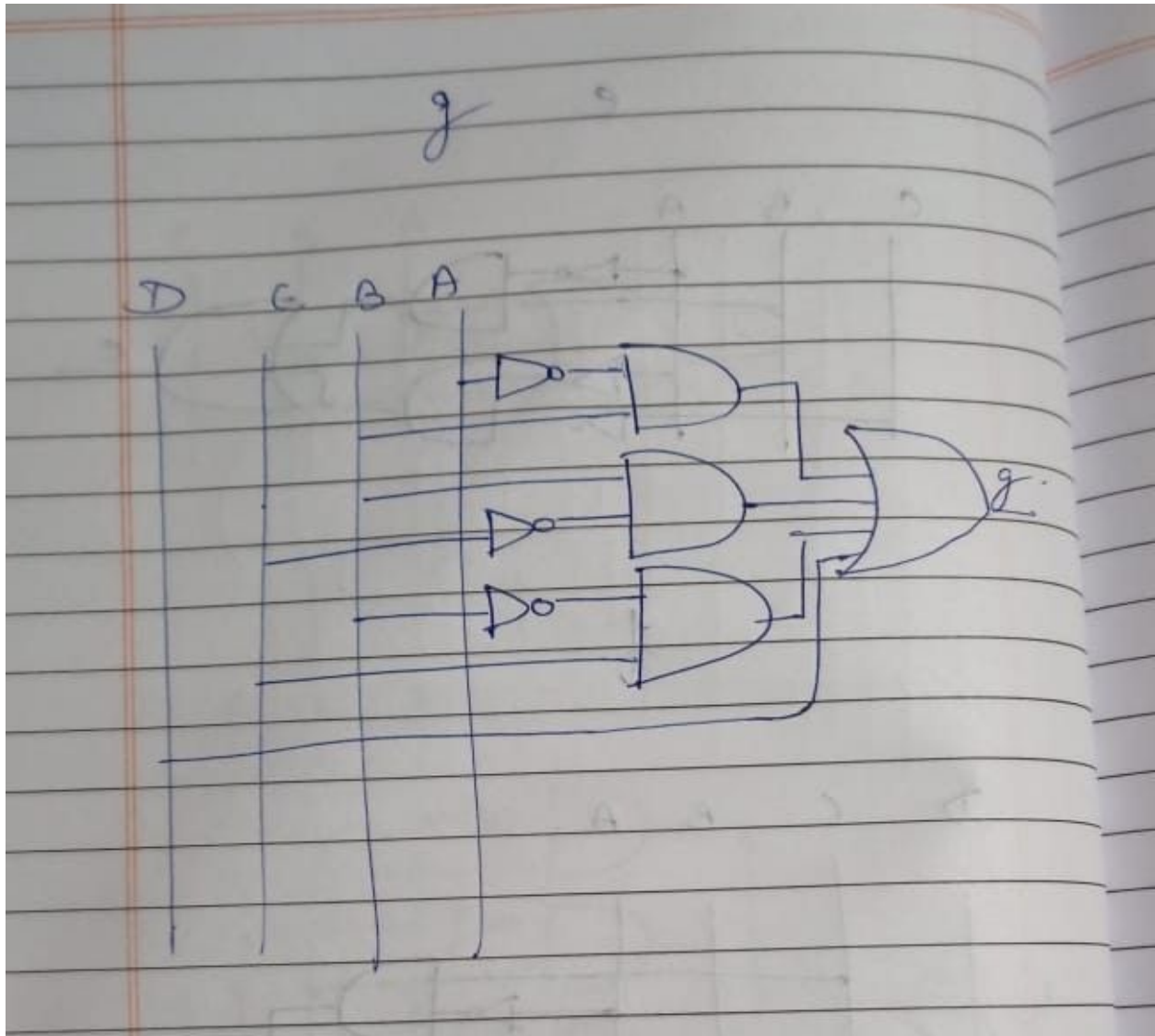

**Truth Table :**

DE	D	C	B	A	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1

5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	0	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	0	1	1

### Observations :

The above experiment depicts how to make a seven segment display by using only AND,OR,NOT gates.

From this we can assume that the above circuit shows the inner workings of a 7 Segment decoder.