

ECE111|Digital Circuits

Dr. Vish Visweswaran

Lab_9:

Student Name : Shivam Agarwal

Roll No. : 2020123

Date : 04/4/2021


AIM 1 : Binary Ripple Counter



Components Used : 1 power supply , 4 resistors , 4 LEDs , 1 slide switches, 2 Dual J-K flip-flop(74HC73) , 1 Square Function Generator

TinkerCad Link :


<https://www.tinkercad.com/things/iqusvdx1kl1-binary-ripple-counter/editel?sharecode=4e25R62SIz2niTLc6WE7ceWH84dmcCmMkqC6HgvD0YA>

Screenshots :

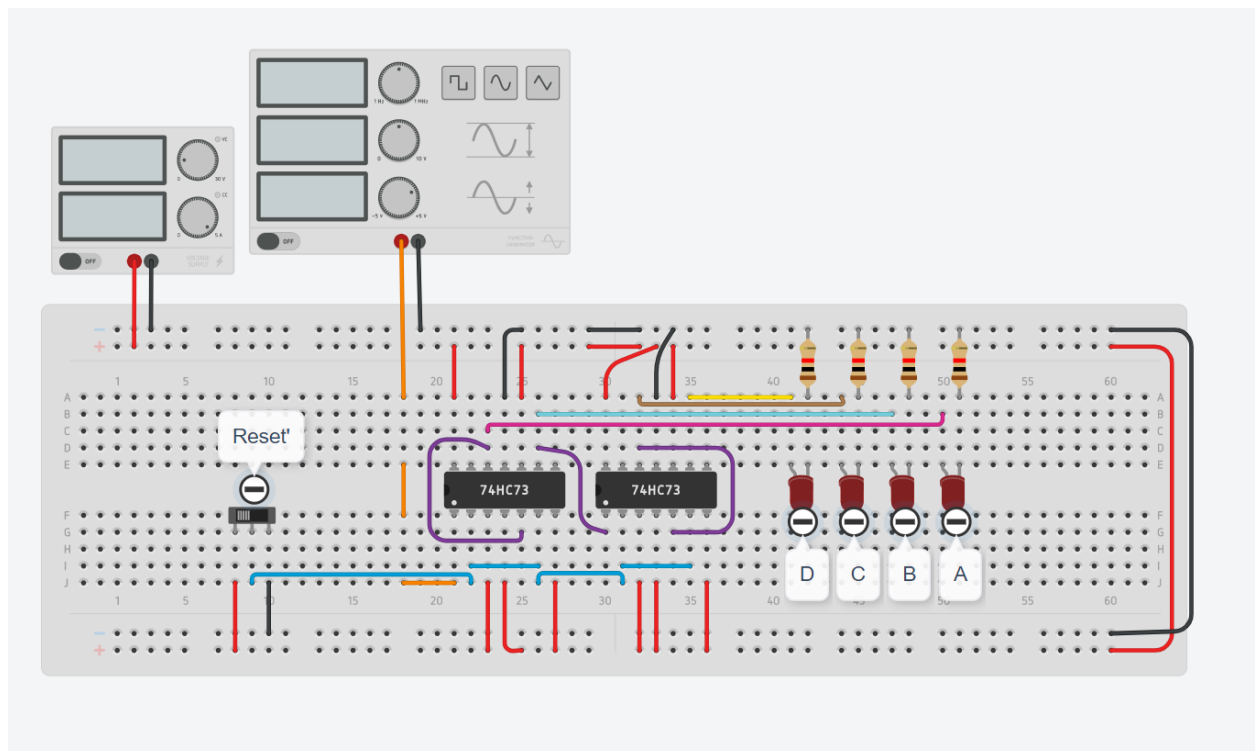

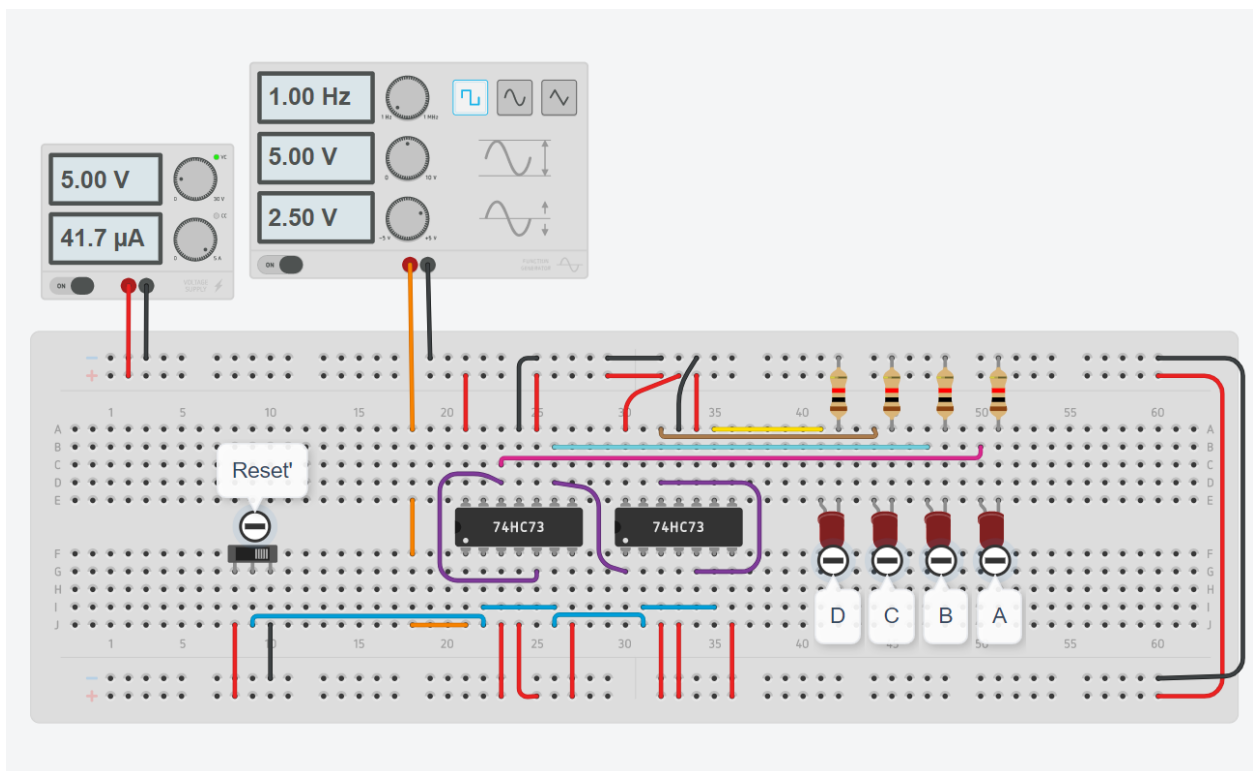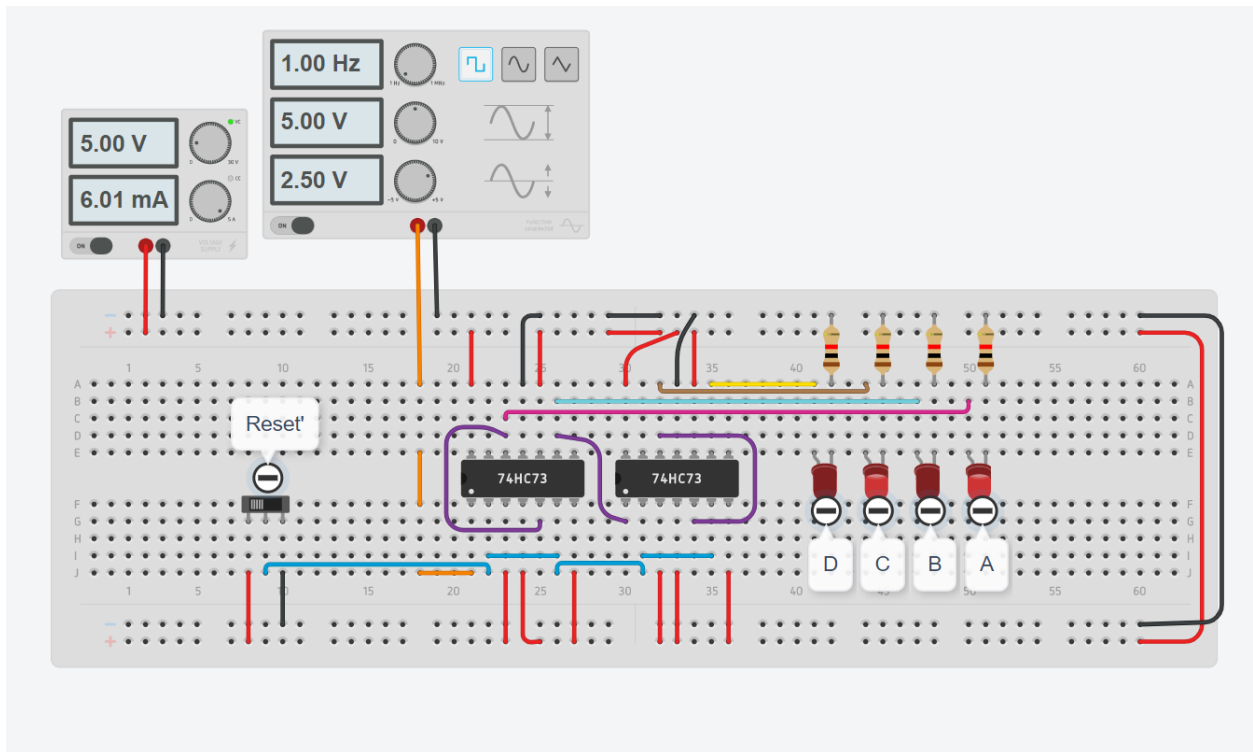

Circuit Diagram :

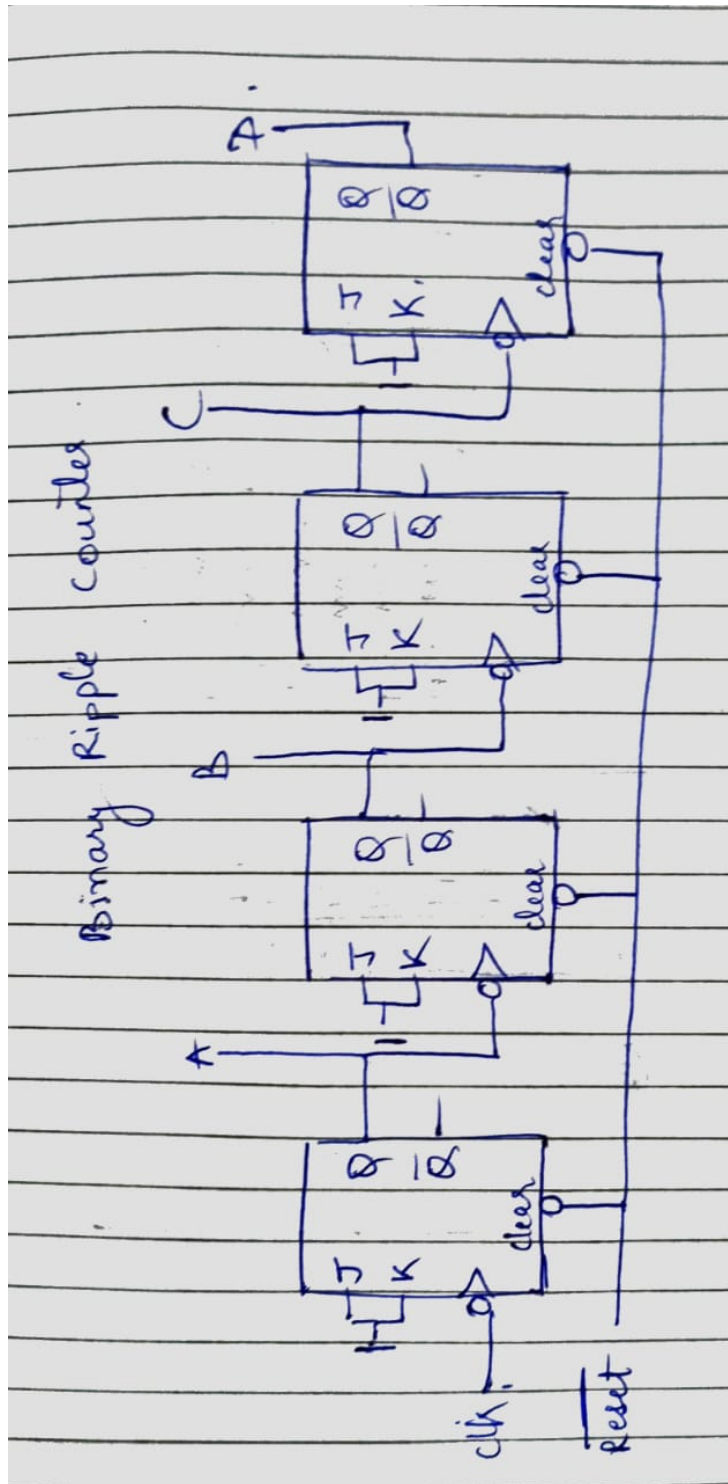

Truth table :

Decimal	D	C	B	A
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	1	1	0	0
13	1	1	0	1
14	1	1	1	0
15	1	1	1	1

Observations :

The circuit acts as a binary up counter and counts numbers from 0 to 15 using JK flip-flops. After counting upto 15 the counter goes back to 0 and starts counting again.

When the value of reset switch is given 0 then the value of the counter resets and counting starts again from 0.

Applications :

1. It can be used as frequency dividers with some changes
 2. It can be used in time measurement for calculating time in timers.
-


AIM 2 : Decade Ripple Counter



Components Used : 1 power supply , 7 resistors , 2 Dual D flip-flop(74HC74) , 1 Square Function Generator , 1 7-segment Decoder , 7 segment display ,1 Quad Nand Gate

TinkerCad Link :



<https://www.tinkercad.com/things/2UPyZJEbHPd-copy-of-binary-ripple-counter/ditel?sharecode=gAeUemVqyhIjIKwrrQ3n2bp-ay0tjHe5U-BM6PJzk5c>

Screenshots :

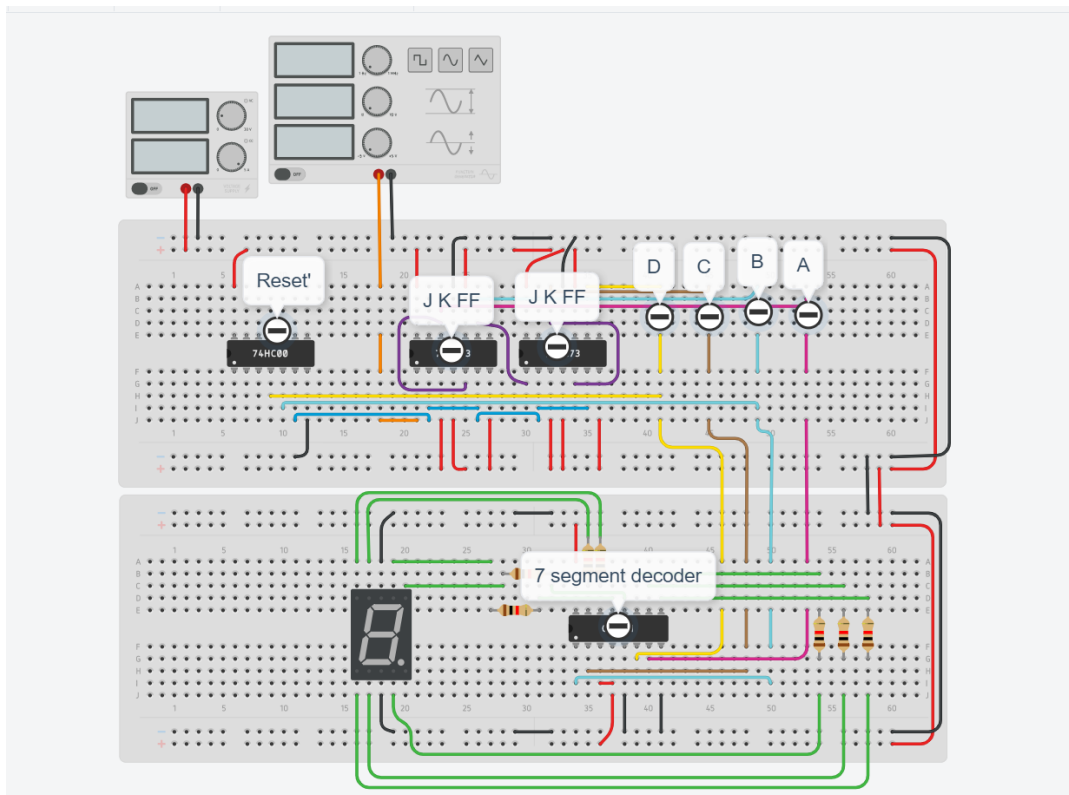

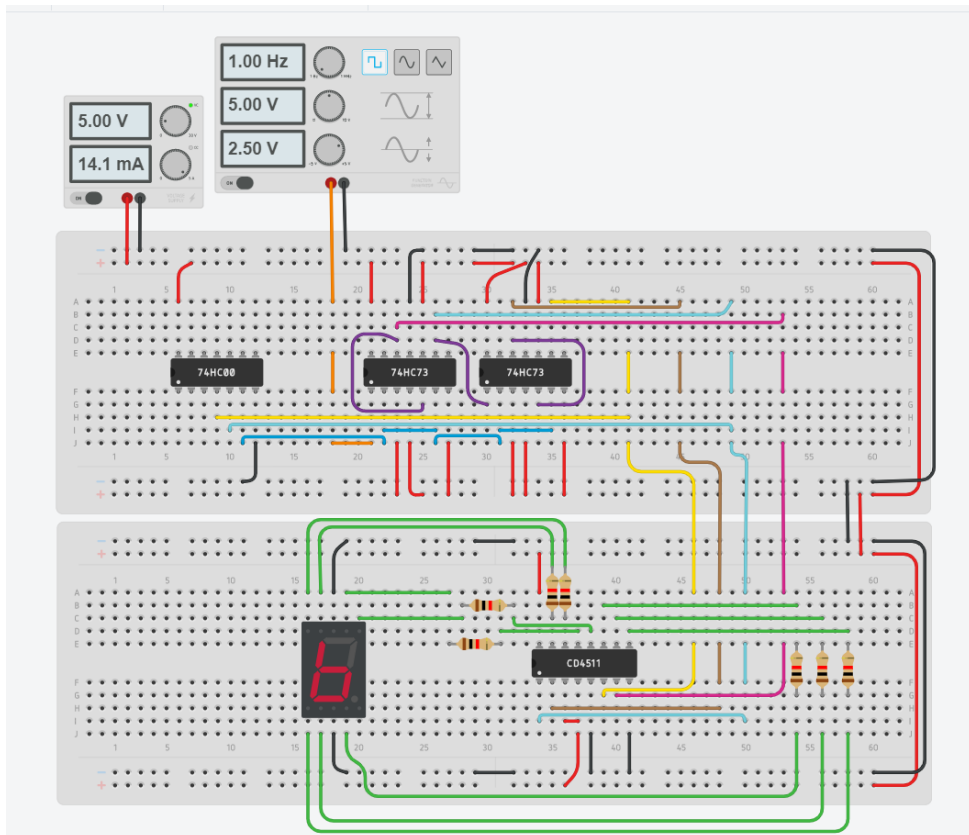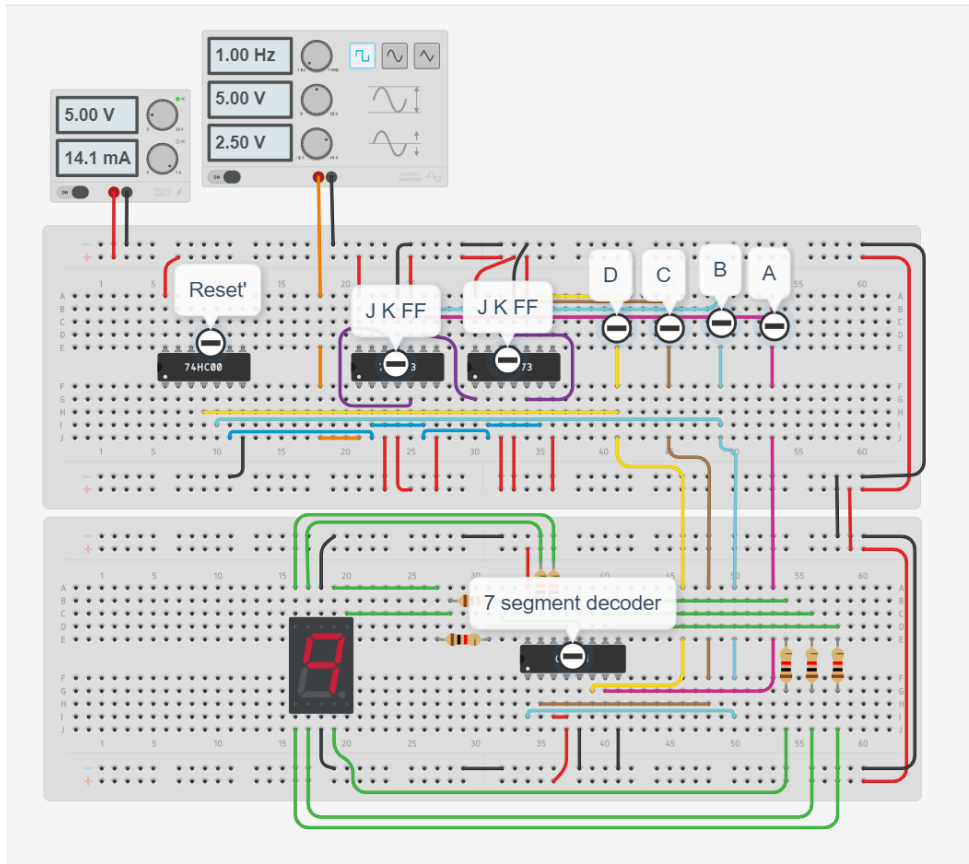

Circuit Diagram:

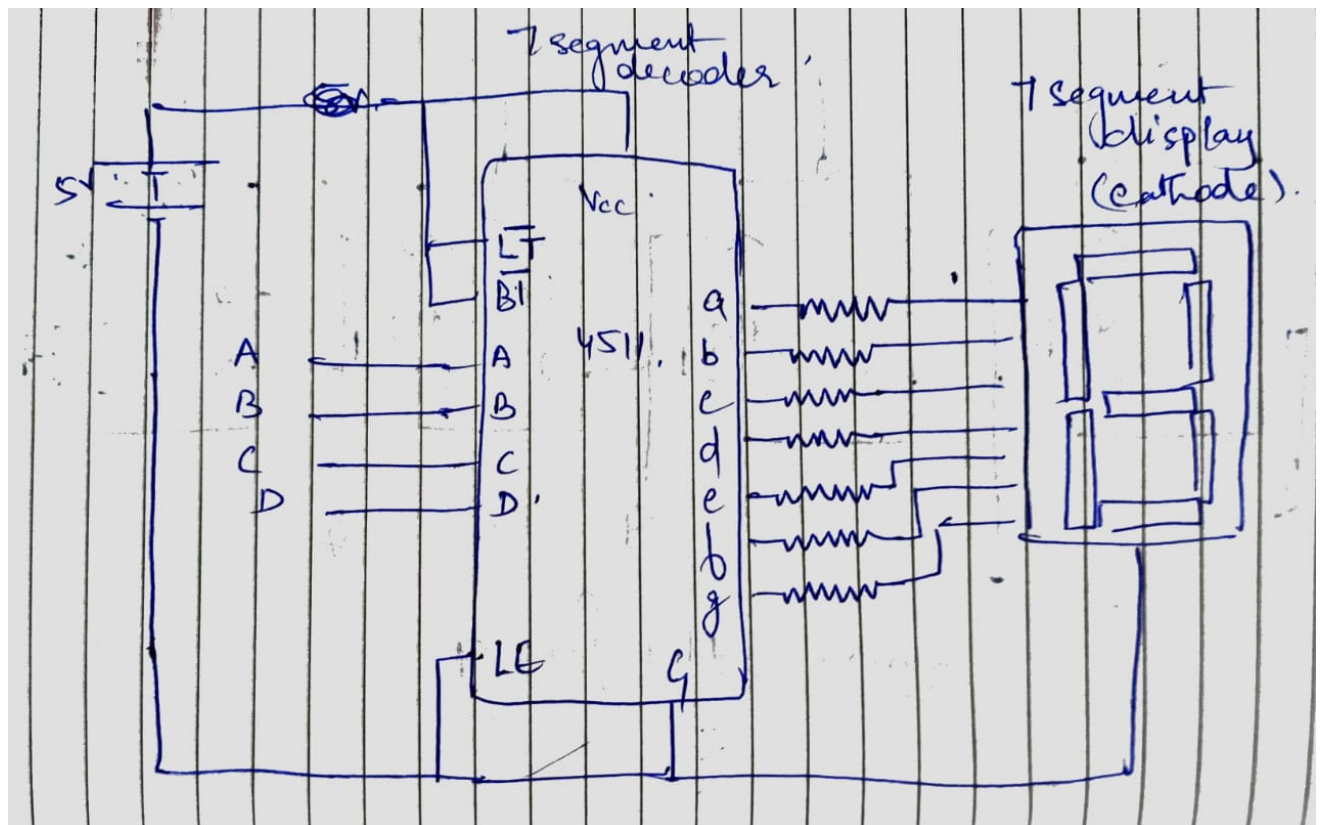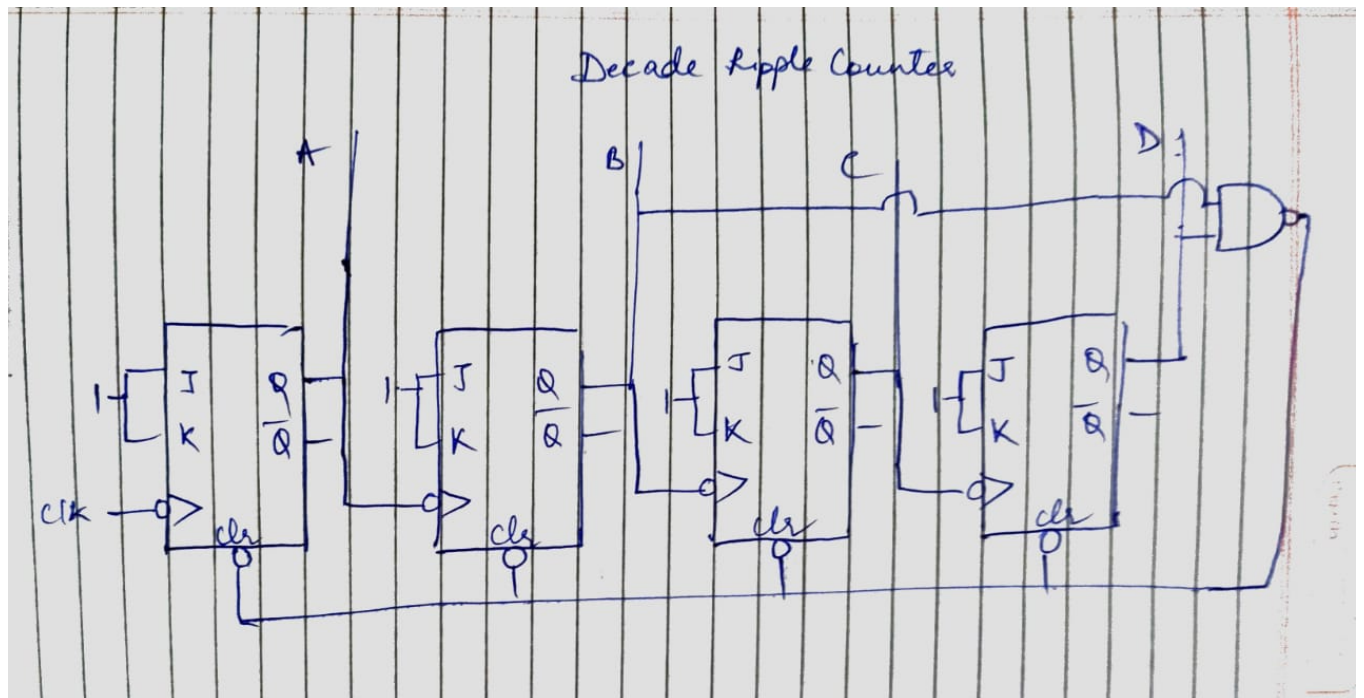

Truth Table :

<u>Output</u>	<u>D</u>	<u>C</u>	<u>B</u>	<u>A</u>
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
0	0	0	0	0
...

Observations :

The Decade ripple counter acts as a binary up counter and counts numbers from 0 to 9 using JK flip-flops. After counting upto 9 the counter goes back to 0 and starts counting again.

When the output of the flip flops becomes 10 or 1010(DCBA) then the value of the reset switch becomes 0 and the counter restarts from 0

Applications :

1. They are used in clock circuits for time measurement.
2. They are used in frequency dividers.